



VIT

Vellore Institute of Technology
(Approved to be University under section 3 of UGC Act, 1956)

Reg.No.:

Slot: B2 + TB2

SCHOOL OF ELECTRONICS ENGINEERING
CONTINUOUS ASSESSMENT TEST - I
FALL SEMESTER 2025-2026

Programme Name & Branch : M. Tech – Embedded Systems
Course Code and Course Name : MAEDS506 - System Design using FPGA
Faculty Name(s) : Dr VIDHYAPATHI CM
Class Number(s) : VL2025260105662
Date of Examination : 18/8/25
Exam Duration : 90 minutes
Maximum Marks: 50

General instruction(s):

• **Answer All Questions**

CO1 - Develop and simulate combinational circuits using HDL and test benches.

CO2 - Develop and simulate sequential circuits using HDL and test benches.

Q. No	Question	M	CO	BL
1.	Evaluate and contrast the following hardware platforms for embedded system development, considering factors such as execution methodology, performance, power efficiency, cost, ease of prototyping, time to market, and other relevant metrics. a) FPGA b) CPU c) ASIC d) GPU	10	CO1	2
2.	Discuss the following concepts in the context of system design using FPGA technology: a) The architecture of Zynq devices and the design flow for embedded systems b) The role of software reference designs and software profiling technique c) The principles of hardware-software co-design and methods for achieving hardware acceleration d) The distinction between hard-core IP and soft-core IP in FPGA-based systems	10	CO1	2
3	Develop a VHDL code and Testbench for an 8:1 MUX using the following modelling techniques. a) Concurrent b) Sequential	10	CO2	3
4.	Develop a VHDL code for an 4:16 Decoder using 2:4 Decoder.	10	CO1	3



VIT

Vellore Institute of Technology
(Deemed to be University) under section 3 of UGC Act, 1956

Reg.No.:

Slot: B2 + TB2

SCHOOL OF ELECTRONICS ENGINEERING
CONTINUOUS ASSESSMENT TEST - I
FALL SEMESTER 2025-2026

5.	Develop a VHDL code to model the below 4-bit adder/subtractor circuit using Structural modelling.	10	CO1	3
----	---	----	-----	---



VIT

Vellore Institute of Technology
(Deemed to be University under section 3 of UGC Act, 1956)


Reg.No.:

Slot: B2 + TB2

SCHOOL OF ELECTRONICS ENGINEERING
CONTINUOUS ASSESSMENT TEST - II
FALL SEMESTER 2025-2026

Programme Name & Branch	: M. Tech – Embedded Systems	
Course Code and Course Name	: MAEDS506 - System Design using FPGA	
Faculty Name(s)	: Dr. VIDHYAPATHI CM	
Class Number(s)	: VL2025260105662	
Date of Examination	: 06/10/25	
Exam Duration	: 90 minutes	Maximum Marks: 50
General instruction(s):		

- Answer All Questions
- CO2 - Develop and simulate sequential circuits using HDL and test benches.
- CO3 - Build and integrate IP cores for an FPGA based system.

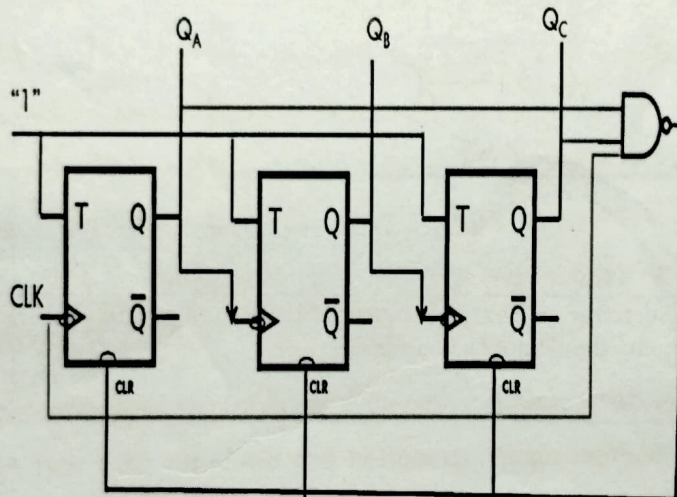Q. No	Question	M	CO	BL										
1.	<p>Model a 3-bit asynchronous mod-6 up counter using VHDL and display the count value in SEVEN SEGMENT display.</p> 	10	CO3	2										
2.	<p>Using VHDL, model a single Frequency Divider which accepts 50 MHz frequency and generates the following OUTPUT frequencies based on the INPUT selector as given in the below table.</p> <table><tr><th>INPUT selector</th><th>OUTPUT</th></tr><tr><td>0</td><td>25 MHz</td></tr><tr><td>1</td><td>50 KHz</td></tr><tr><td>2</td><td>5 KHz</td></tr><tr><td>3</td><td>500 Hz</td></tr></table>	INPUT selector	OUTPUT	0	25 MHz	1	50 KHz	2	5 KHz	3	500 Hz	10	CO2	2
INPUT selector	OUTPUT													
0	25 MHz													
1	50 KHz													
2	5 KHz													
3	500 Hz													




VIT

Vellore Institute of Technology
(Deemed to be University under section 3 of UGC Act, 1956)

Reg.No.:

Slot: B2 + TB2

SCHOOL OF ELECTRONICS ENGINEERING
CONTINUOUS ASSESSMENT TEST - II
FALL SEMESTER 2025-2026

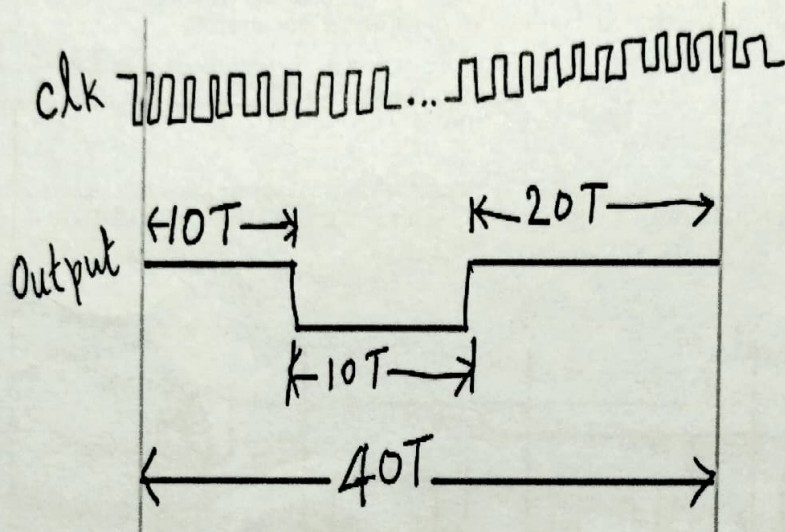3	Develop a state machine for a Water Vending Machine which should accept ₹5, ₹10, ₹20 Rupee Coins/Notes and dispense 1 liter of water for ₹25 Rupee. The Vending machine should refund the extra money if any. Model the State Machine using VHDL code.	10	CO2	3
4.	<p>Generate the following Output signal which changes only during positive edge using Finite State Machine (FSM) based VHDL programming approach. T is the basic one clock period.</p>  <p>The diagram shows a clock signal (clk) and an output signal. The output signal is a square wave that changes only at the positive edges of the clock. The output is high for 10T, low for 10T, and high for 20T, with a total period of 40T.</p>	10	CO2	3
5.	Model a string detector to detect the sequence "10101" using VHDL. Note: Overlapping should not be considered.	10	CO2	3


VIT

Vellore Institute of Technology
(Approved by the Council for Higher Education, India, Dec. 1998)
Final Assessment Test – November 2025

Course: MAEDS506 - System Design using FPGA

Class NBR(s): 5661

Time: Three Hours

Slot: B2+TB2

Max. Marks: 100

- KEEPING MOBILE PHONE/ANY ELECTRONIC GADGETS, EVEN IN 'OFF' POSITION IS TREATED AS EXAM MALPRACTICE
- DON'T WRITE ANYTHING ON THE QUESTION PAPER

COs	CO Statements
CO1	Develop and simulate combinational circuits using HDL and test benches.
CO2	Develop and simulate sequential circuits using HDL and test benches.
CO3	Build and integrate IP cores for an FPGA based system.
CO4	Apply a hardware-software co-design approach to accelerate real-world applications.
CO5	Simulate an IP-based system design using an FPGA.

BL – Blooms Taxonomy Level (1 – Remember, 2 – Understand, 3 – Apply, 4 – Analyse, 5 – Evaluate, 6 – Create)

Answer ALL Questions

(10 X 10 = 100 Marks)

- Compare and contrast the execution models of Field Programmable Gate Arrays (FPGAs) and traditional processor-centric architectures such as CPUs and microcontrollers. Discuss how parallelism is achieved in FPGAs and how it differs from the sequential or limited parallel execution in CPUs and microcontrollers. Highlight the implications of these models on important metrics of system design. CO4 BL3
- Map the embedded system design cycle onto a modern FPGA architecture. Explain how both top-down and bottom-up design methodologies are applied within this context. Highlight the advantages, challenges, and typical use cases of each approach in FPGA-based embedded system development. CO4 BL3
- (i) Given the following part of VHDL code, fill in the table. [5] CO1 BL3

SIGNAL a: BIT;

SIGNAL b: BIT_VECTOR (7 DOWNT0 0);

SINGAL c: STD_LOGIC;

SIGNAL d: STD_LOGIC_VECTOR (7 DOWNT0 0);

SIGNAL e: INTEGER RANGE 0 TO 7;

OPERATION	Legal/Illegal
$e \leq d;$	
$d(0) \leq c;$	
$a \leq b(5);$	
$b \leq d;$	
$b(0) \leq a;$	

(ii) Tabulate the differences between WHEN and CASE.

[5]

4. Model the carry ripple adder given in Fig.1. in VHDL with the following style

CO1 BL3

a) Using **loop** VHDL construct

[5]

b) Using **generate** VHDL construct

[5]

 


Fig.1. Carry Ripple adder

5. Develop a VHDL code to model a 64-bit Arithmetic and Logical Unit(ALU) as shown in Fig.2.

CO1 BL4

 


Fig.2. ALU

6. Write a Structural VHDL code to model Tapped delay line given below in Fig.3.
Note: 4-Stage SR means 4-bit SHIFT REGISTER.

 


Fig.3. Tapped delay

- 7.(a) Develop a VHDL code to model the given Traffic Light Controller in Fig.4.
Assume the clock frequency is 60 Hz.

 


Fig.4. Traffic Light Controller

OR

- 7.(b) Develop a VHDL code to generate the following **outp** waveform given in Fig.5.

 


Fig.5. outp waveform

- 8.(a) Develop a VHDL code to implement a progressive 2-digit decimal counter ($0 \rightarrow 99 \rightarrow 0$), with external asynchronous reset. Also map the binary coded decimal (BCD) output to seven segment display (SSD).

CO4 BL4

OR

- 8.(b) Generate the following Output signal as shown in Fig.6 using Finite State Machine (FSM) based VHDL programming approach where T_0 is the basic one clock period. Assume the clock frequency is 1 Hz and map the output to an LED.

CO4 BL4

 


Fig.6. output waveform

9. (i) Explain the concept of Hardware acceleration and Partial Reconfiguration in FPGA design. [5] CO5 BL3
- (ii) Explain the roles of bitstream encryption and tamper detection mechanisms in protecting FPGA-based systems from unauthorized access and physical attacks. [5]
10. Assume a design in which it has a mixed FPGA + ARM SoC system where custom hardware logic in the FPGA Programmable Logic (PL) must be controlled and accessed by software running on the ARM Processing System (PS). The communication is to be handled via AXI interconnects. CO3 BL3
- (i) Describe the role and types of AXI interfaces (AXI4, AXI4-Lite, AXI4-Stream) in such a system.
- (ii) Outline how to package a custom IP (hardware module) so that it can be accessed via AXI from the ARM side (i.e. how to wrap your logic). What are the key interface signals and metadata attributes needed?

⇔⇔⇔ T/K/TY ⇔⇔⇔